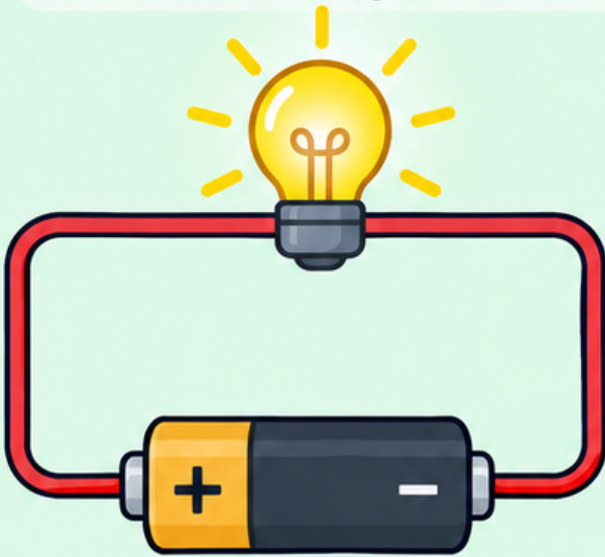


Electricity & Circuits

Complete the path


1 Closed Circuit

Complete path, current flows, bulb lights.



2 Open Circuit

Broken path, no flow, bulb off.

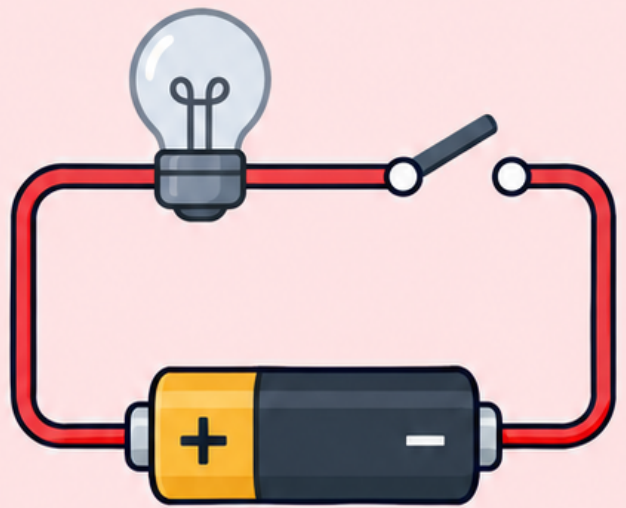

3 Conductors

Metal wires allow electricity to flow.



Metal wire




Metal

4 Insulators

Rubber, plastic, and wood stop electricity from flowing.



Rubber

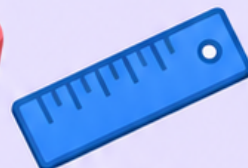

Plastic



Wood




A bulb lights only when the circuit makes a complete loop.

Electricity & Circuits

Complete the path


1 Closed Circuit

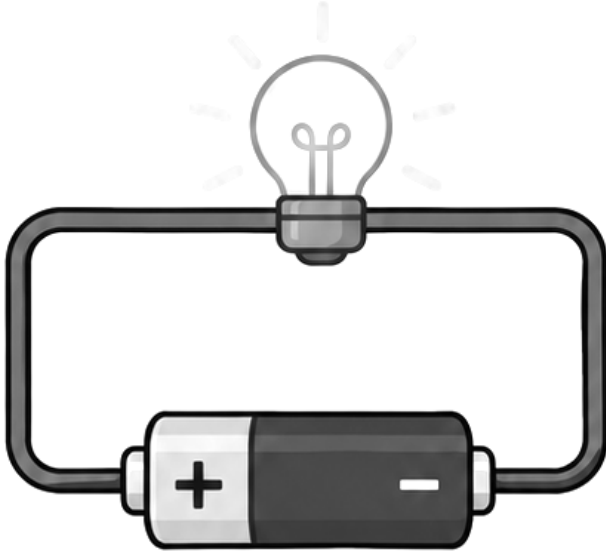Complete path, current flows,
bulb lights.



2 Open Circuit

Broken path, no flow,
bulb off.

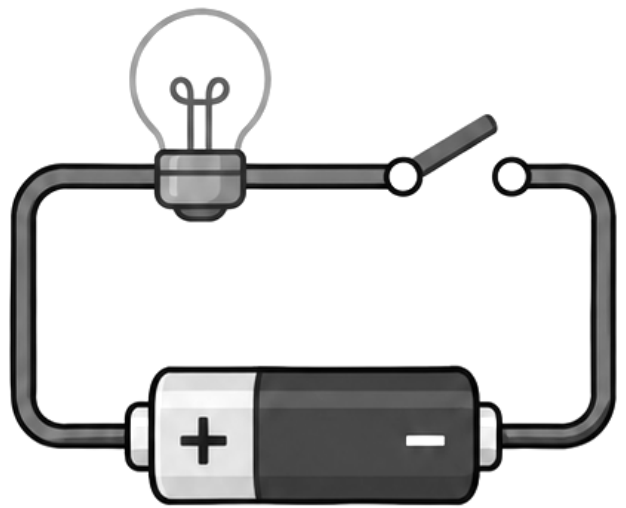

3 Conductors

Metal wires allow
electricity to flow.




Metal wire



Metal

4 Insulators

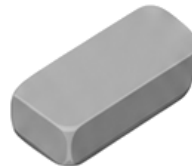
Rubber, plastic, and wood
stop electricity from flowing.



Rubber



Plastic

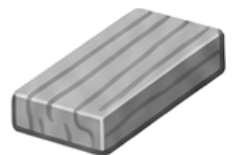

Wood



**A bulb lights only when the circuit
makes a complete loop.**